
 


Power Consumption


SPECIAL TOPIC 2

Load Capacitance of a Gate

 

$$C_L = \underbrace{C_{n1}}_{\text{wire cap}} + \underbrace{C_{U2/B} + C_{U3/D}}_{\text{pin cap}}$$

Switching Activity: Charge Flow

 

**Low-to-High
(L-H)**

**High-to-Low
(H-L)**

**Pulse (L-H +
H-L)**

- $Q = C_L V_{dd}$
- For every pulse, charge Q flows from VDD to GND

Switching Activity: Power Dissipation

- Energy dissipated for every pulse, when charge Q flows from V_{DD} to GND:

$$E = QV_{dd} = (C_L V_{dd})V_{dd} = C_L V_{dd}^2$$

- Power is energy dissipated per second.
- If there are n_p pulses per second at a gate's output, switching power dissipation of the gate is:

$$P = C_L V_{dd}^2 n_p$$

Switching Power for Clocks & Data

- For a clock with frequency f , $n_p = f$
 - Switching power dissipation of a buffer driving clock is:

$$P = C_L V_{dd}^2 f$$

- For data signals, we define an activity factor, α :

$$\alpha = n_p / f$$

- Switching power for driver of such a signal is:

$$P = C_L V_{dd}^2 f \alpha$$


- Generally, $\alpha \ll 1$ and clock is the most active signal in the circuit

Clock Gating

SPECIAL TOPIC 3

Clock Gating

 
64-bit register which changes state only when some enable signal, EN, is high:




Circuit without Clock Gating



 
Rising edges of these two pulses do no work since E is low \Rightarrow pulses can be eliminated to save power





Circuit with Clock Gating

 

**GCLK: gated
clock**

 

 
 
Problem with using AND gate for clock gating



- If EN changes when CLK is high, we get incorrect clock edges:
 - Cannot let EN change when CLK is high

Integrated Clock Gating Cell (ICG)

 
 
- Cannot let EN when CLK is high: use latch (level-sensitive) to block EN when CLK is high
 - Latch is transparent when CLK is low
- Combination of latch and AND gate is called an “Integrated Clock Gating” cell (ICG)



- EN does not go through to the AND gate when CLK is high
 - Latch is transparent with CLK is low

ICG with Test Feature

  
- When chip is being tested, clock must be ungated regardless of value of EN
 - Add “test” input (T) to ICG to bypass EN during test:




- $T = 1$ when circuit is being tested
- ICG is transparent to CLK when $T = 1$, regardless of value of EN

Symbol for ICG

 - There is no standard symbol for an ICG
- We will use the following as symbols for ICGs in this class:




**ICG without test
input**

 


**ICG with test
input**

ICGs in Standard Cell Libraries

 
- Most standard cell libraries contain ICGs
- In the dotlib, ICGs, and only ICGs, must have the attribute “clock_gating_integrated_cell” defined



 clock_gating_integrated_cell : latch_posedge;



 clock_gating_integrated_cell :
latch_posedge_precontrol;



clock_gating_integrated_cell :
latch_posedge_postcontro
l;